



# BSV Training



## Eg04: Microarchitectures: FSMs and Pipelines

Using a “dynamic shifter” as an example, we illustrate how BSV rules can be used to express common microarchitecture structures: iterative, rigid-pipelined and elastic-pipelined.

```

import PIP004;
typedef Bit2(24) (out0);
module ex_hdl_csrR_in[empty];
  Integer nfa_depth = 16;
  function Bit2(24) dynamic_shift(Bit2(24) in);
    return (in >> 1);
  endfunction
  PIP004(in0) in0_bound;
  subP004(PIP004(nfa_depth)) in0_bound(in0_bound);
  PIP004(in0_bound) out0_bound;
  subP004(PIP004(nfa_depth)) in0_bound(out0_bound);
  PIP004(in0_bound) out0_bound;
  subP004(PIP004(nfa_depth)) in0_bound(out0_bound);
  rule exp1 (True);
    out0 <- in0;
    PIP004(in0) out0_bound;
    out0_bound <- in0;
    out0_bound <- in0;
  endrule;
endmodule

```

 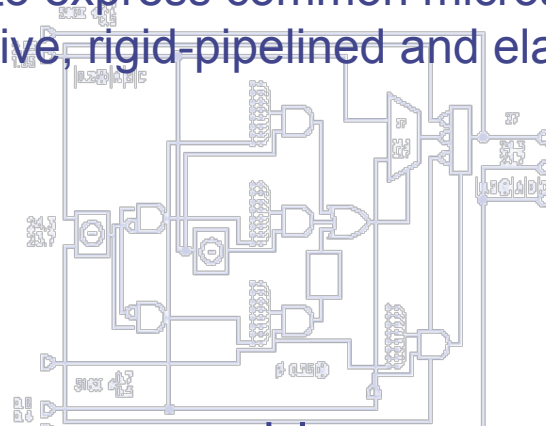


[www.bluespec.com](http://www.bluespec.com)

# Dynamic shifts

- Goal: circuit to implement a left-shift by a dynamic amount:  $z = \text{shift}(x, y)$   
i.e.,  $z = x$  left-shifted by  $y$  positions, where  $y$  is dynamic (run-time value)
- Algorithm: a dynamic shift can be achieved as a composition of static shifts corresponding to each bit of  $y$ .
- Example: Suppose  $y$  has type Bit #(3)
  - $\text{shift}(x, y) =$ 

shift $x$ by 1 ( $= 2^0$ )	if $y[0] == 1$
and by 2 ( $= 2^1$ )	if $y[1] == 1$
and by 4 ( $= 2^2$ )	if $y[2] == 1$
- Note: shifting by constant  $2^j$  is trivial: just a “lane change” using only wires, no gates:

 

## Example variations

The accompanying code demonstrates six variations:

- The following are in Eg04a\_MicroArchs/src\_BSV/. Each shifts an 8-bit value  $x$  by a 3-bit value  $y$ .

Shifter_iterative.bsv	Sequential, iterative
Shifter_pipe_rigid.bsv	Pipelined. Rigid ("synchronous", assumes no gaps in data stream)
Shifter_pipe_elastic.bsv	Pipelined. Elastic ("asynchronous", accommodates gaps in input stream)

- The following are in Eg04b\_MicroArchs/src\_BSV/. They are generalizations of the previous three, such that each shifts an  $n$ -bit value  $x$  by a  $\log(n)$ -bit value  $y$ . The testbench demonstrates instances where  $n = 16$

Shifter_iterative.bsv	... ditto ...
Shifter_pipe_rigid.bsv	... ditto ...
Shifter_pipe_elastic.bsv	... ditto ...

# Building and running the codes

Each variation is built and run in the same way:

- In the “src\_BSV” directory, create a symbolic link from “Shifter.bsv” to the variation of interest. E.g.,

```
% ln -s -f Shifter_iterative.bsv Shifter.bsv
```

- In the Build directory you can use the ‘Makefile’ for building and running Bluesim or Verilog sim:

```
% make compile link simulate           // for Bluesim
% make verilog v_link v_simulate       // for Verilog sim
```

# Interface for the shifter(s)

All three variations of the shifter have the same interface (see file Shifter\_IFC.bsv):

```
typedef Server #(Tuple2 #(Bit #(8), Bit #(3)),  
                  Bit #(8))  
    Shifter_IFC;
```

This is an example of a common BSV practice—to re-use “standard” interfaces already provided in the BSV library, rather than defining new, *ad hoc* interfaces for each new module:

```
interface Server #(t1, t2);  
    interface Put #(t1) request;  
    interface Get #(t2) response;  
endinterface
```

(from the ClientServer library)

```
interface Put #(t1);  
    method Action put (t1 x);  
endinterface
```

```
interface Get #(t2);  
    method ActionValue #(t2) get ();  
endinterface
```

(from the GetPut library)


*Note: these are similar to interfaces in the SystemC TLM 2.0 library*

Our interface `Shifter_IFC` will therefore have

- a `request.put` method by which the environment can send a 2-tuple input
  - The 2-tuple is a pair of values, 8 bits (for x) and 3 bits (for y)
- a `response.get` method by which the environment can receive an 8 bit output

 
# Sequential, iterative shifter

File: Eg04a\_MicroArchs/src\_BSV/Shifter\_iterative.bsv



The FSM (and its actions) is implemented using 3 BSV rules
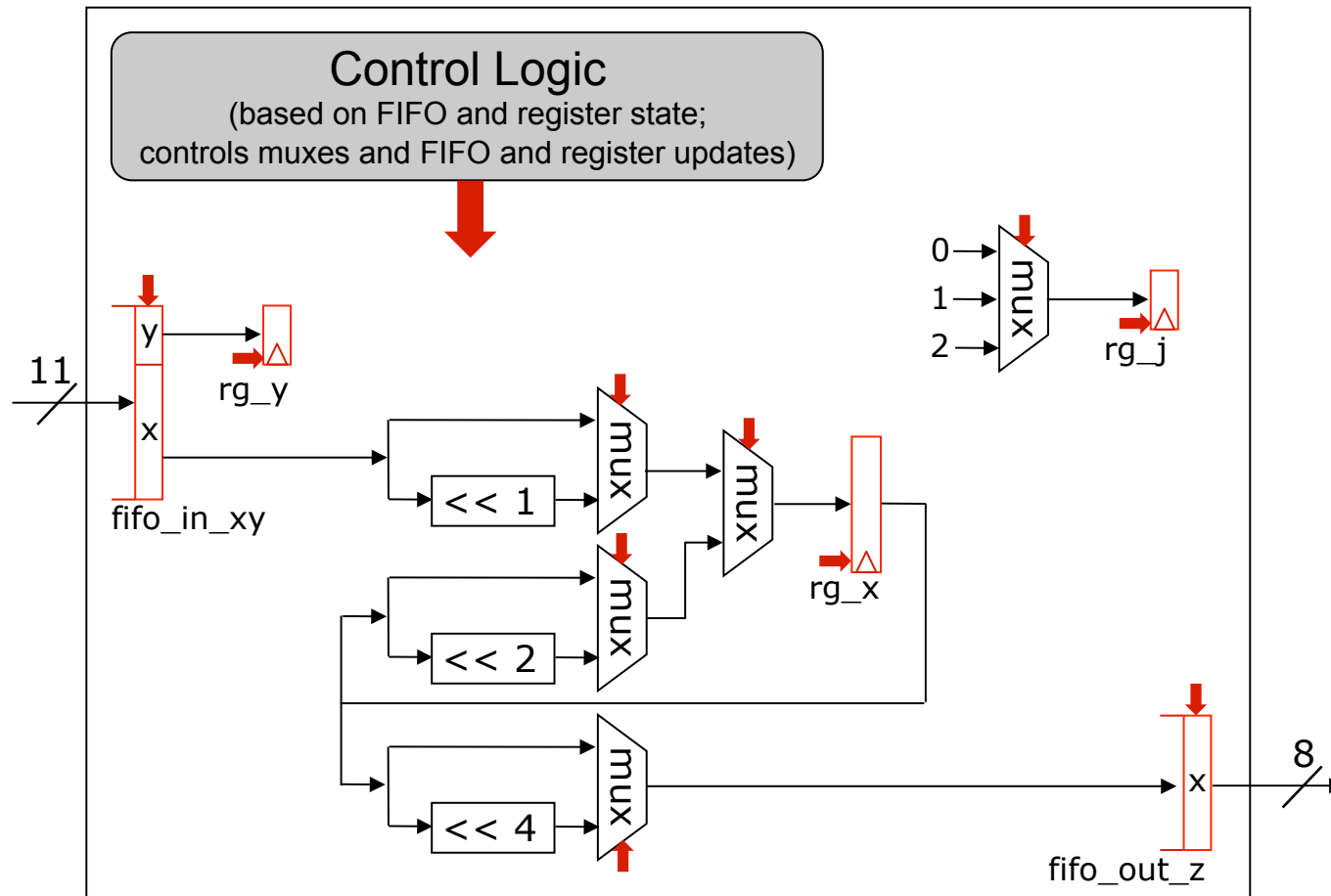
# Sequential, iterative shifter: more detail



*The Control Logic is automatically compiled by bsc from the BSV rules*

# A testbench to drive the shifter module

File: Eg04a\_MicroArchs/src\_BSV/Testbench.bsv

```
module mkTestbench (Empty);
  Shifter_Ifc shifter <- mkShifter;

  Reg #(Bit #(4)) rg_y <- mkReg (0);

  rule rl_gen (rg_y < 8);
    shifter.request.put (tuple2 (8'h01, truncate (rg_y))); // or rg_y[2:0]
    rg_y <= rg_y + 1;
  endrule

  rule rl_drain;
    let z <- shifter.get_z.get ();
    $display ("Output = %8b", z);
    if (z == 8'h80) $finish ();          // 8'b10000000
  endrule
endmodule: mkTestbench
```

*rl\_gen sends in the following inputs:*

```
00000001  0
00000001  1
00000001  2
...
00000001  7
```

*rl\_drain should show the following outputs:*

```
00000001
00000010
00000100
...
10000000
```

*(The same testbench will be used for all three versions of the shifter)*



## Build and run, using the iterative shifter

- In the “src\_BSV” directory, create a symbolic link from “Shifter.bsv” to the variation of interest:

```
% ln -s -f Shifter_iterative.bsv Shifter.bsv
```

- In the upper directory (Eg04a\_MicroArchs or Eg04b\_MicroArchs), build and run either using BDW or the ‘make’ commands, either with Bluesim or with Verilog sim, as described earlier
- Verify that the program produces the expected output
- The \$displays on the input and output also print the clock cycle on which each input and output is done
  - Observe that after a start-up transient, input and output occur every 3 cycles. Why?


# Time-out to reinforce some concepts

Please study the lecture: `Lec_Interfaces_TLM` to understand the concepts `Get`, `Put`, `Client` and `Server` interfaces, and the `mkConnection` module.

Please also look at Section 10, “Pattern Matching” in the Reference Guide for more information on the “match” construct.
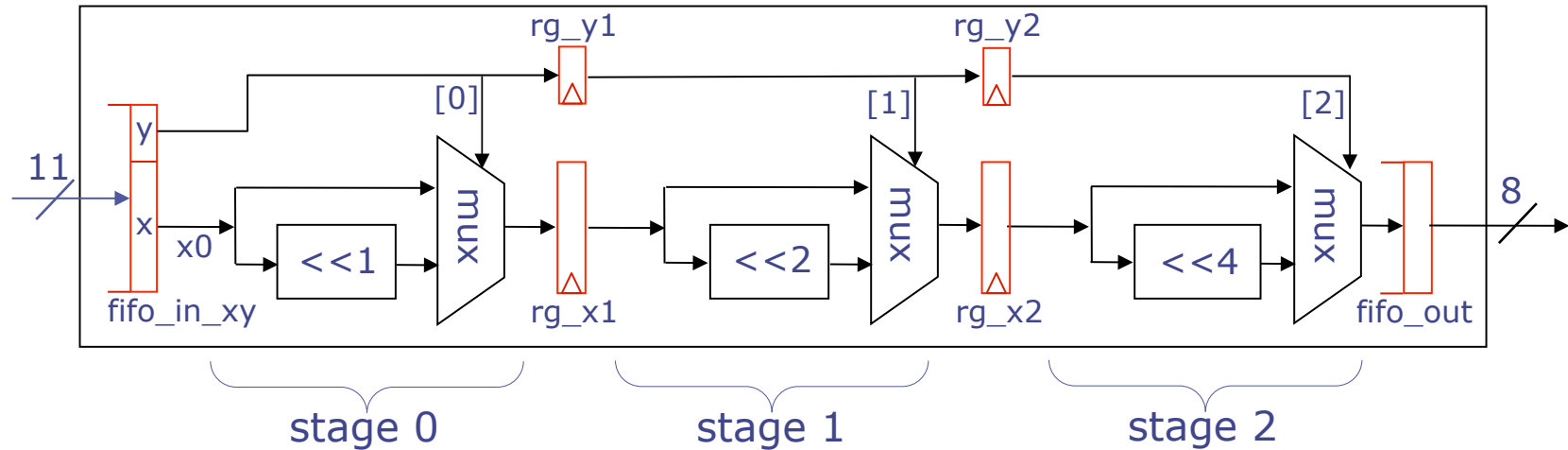
# "Rigid" pipelined shifter

File: Eg02a\_MicroArchs/src\_BSV/Shifter\_pipe\_rigid.bsv



```
rule rl_all_together;
  // Stage 0
  match { .x0, .y0 } = fifo_in_xy.first; fifo_in_xy.deq;
  rg_x1 <= ((y0[0] == 0) ? x0 : (x0 << 1));
  rg_y1 <= y0;

  // Stage 1
  rg_x2 <= ((rg_y1[1] == 0) ? rg_x1 : (rg_x1 << 2));
  rg_y2 <= rg_y1;

  // Stage 2
  fifo_out_z.enq (((rg_y2[2] == 0) ? rg_x2 : (rg_x2 << 4)));
endrule
```

# Build and run, using the rigid pipelined shifter

- In the “src\_BSV” directory, create a symbolic link from “Shifter.bsv” to the variation of interest:

```
% ln -s -f Shifter_pipe_rigid.bsv Shifter.bsv
```

- In the upper directory (Eg04a\_MicroArchs or Eg04b\_MicroArchs), build and run either using BDW or the ‘make’ commands, either with Bluesim or with Verilog sim, as described earlier
- Verify that it is pipelined, i.e., that input and output happen on every clock
- However, the output does not seem to be fully correct:


```
01010101  
10101000  
00000001  
00000010  
00000100  
00001000  
00010000  
00100000
```

ok

*Why?*

*... and then the program hangs*

# “Stranding” in the rigid shifter

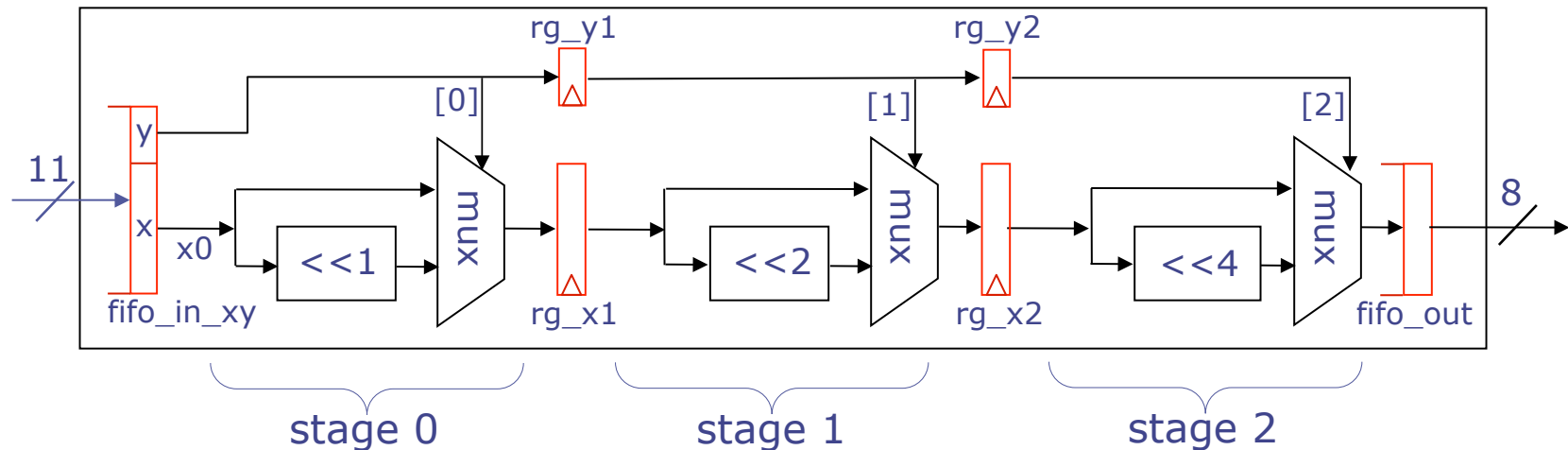

Actually output is:

01010101  
 10101000  
 00000001  
 00000010  
 ...  
 00010000  
 00100000


... and then the program hangs

The first two outputs are just based on the initial unspecified values in rg\_x1, rg\_y1, rg\_x2 and rg\_y2, as they are pushed through the pipeline.  
 bsc usually uses 'hA...A' (10101010...1010) for initial values of unspecified state.

The remaining outputs are the correct outputs, but:

- when rl\_gen stops feeding the input fifos,
- rl\_all\_together can no longer fire (since it invokes fifo\_in\_x.first whose method condition will be false)
- rl\_drain can no longer fire if fifo\_out is empty
- and so the last two values are “stranded” in rg\_x1 and rg\_x2

## Observations about the rigid shifter

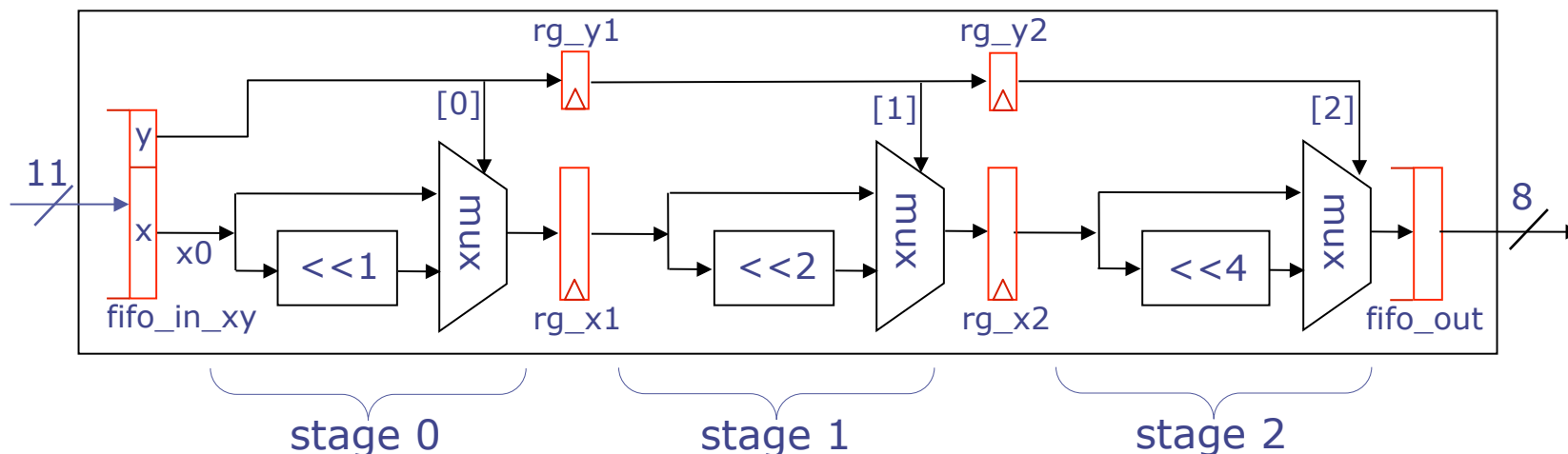


The “rigid” shifter is an example of a simple pipeline implementation that is ok if we have a non-stop, continuous stream of data with no gaps/bubbles. We also call such pipelines “synchronous”, or “lock-step”.

The key observation about the program structure is that all the actions in the pipe are expected to be simultaneous, and therefore placed in a single rule.
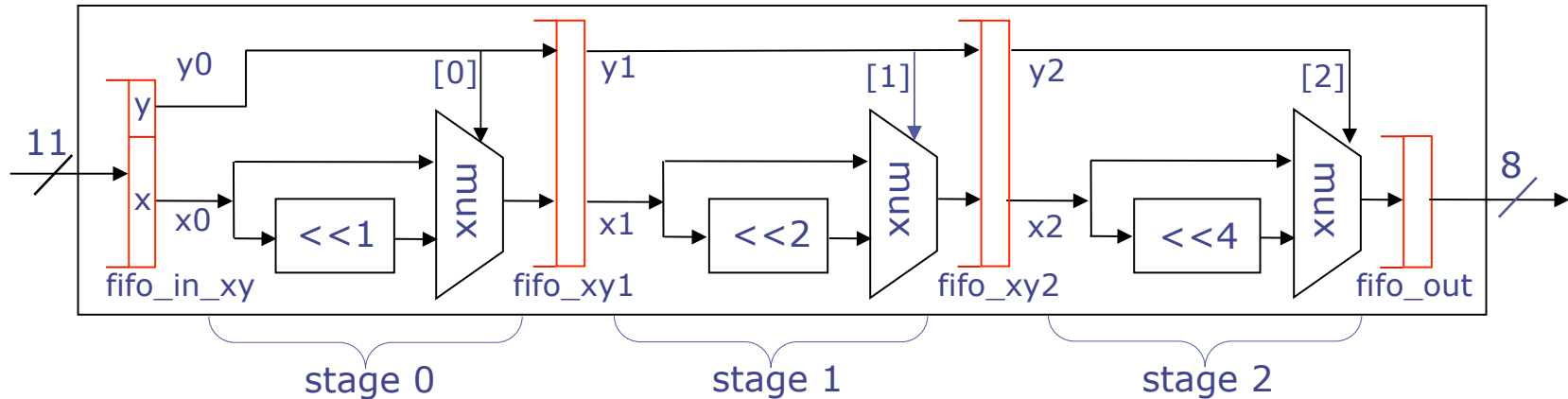
# Elastic, pipelined shifter

File: Eg02a\_MicroArchs/src\_BSV/Shifter\_pipe\_elastic.bsv



```

module mkShifter (Shifter_Ifc);
...
FIFO #(Tuple2 #(Bit #(8), Bit #(3))) fifo_xy1 <- mkFIFO;
FIFO #(Tuple2 #(Bit #(8), Bit #(3))) fifo_xy2 <- mkFIFO;

rule rl_stage0;
  match { .x0, .y0 } = fifo_in_xy.first;  fifo_in_xy.deq;
  fifo_xy1.enq (tuple2 ((y0[0] == 0) ? x0 : (x0 << 1)), y0));
endrule

rule rl_stage1;
  match { .x1, .y1 } = fifo_xy1.first;  fifo_xy1.deq;
  fifo_xy2.enq (tuple2 ((y1[1] == 0) ? x1 : (x1 << 2)), y1));
endrule

rule rl_stage2;
  match { .x2, .y2 } = fifo_xy2.first;  fifo_xy2.deq;
  fifo_out.enq ((y2[2] == 0) ? x2 : (x2 << 4));
endrule
...
endmodule

```

*We now have a separate rule for each stage.*

*Each rule can independently fire if its condition is true.*

## Build and run, using the elastic pipelined shifter

- In the “src\_BSV” directory, create a symbolic link from “Shifter.bsv” to the variation of interest:

```
% ln -s -f Shifter_pipe_elastic.bsv Shifter.bsv
```

- In the upper directory (Eg04a\_MicroArchs or Eg04b\_MicroArchs), build and run either using BDW or the ‘make’ commands, either with Bluesim or with Verilog sim, as described earlier
- Verify that the program produces the expected output
- Verify that it is pipelined, i.e., that input and output happen on every clock



# Summarizing what we've seen so far

- Iterative, rigid-pipelined, and elastic-pipelined structures are three examples of micro-architectural choices for the user.
  - They have different characteristics: area, clock speed, throughput, energy consumption, ...
  - Which one is “best” depends on your design objectives.
- BSV does not (and should not!) make these choices for the user.
  - In creating software, algorithm design is best done by humans (not by programming languages).
  - Similarly, in creating hardware, architectural design is best done humans (not hardware design languages).
  - In both cases, languages can only facilitate quick and reliable expression of the choice made by the human designer, together with efficient implementation.

## Generalizing the dynamic shifters for arbitrary bit-width

Please change directories  
from Eg04a\_MicroArchs/  
to Eg04b\_MicroArchs/

# Time-out to reinforce some concepts

Before moving on with the examples, please study the lecture: `Lec_Types` to understand the concepts behind types, polymorphism, and numeric types.

Please also *skim* through Section C.3 (“Vectors”) in the Reference Guide.

# Generalized interface for the shifters

All three variations of the shifter have the same interface (see file Shifter\_IFC.bsv):

```
typedef Server #(Tuple2 #(Bit #(n), Bit #(TLog #(n))),  
                Bit #(n))  
    Shifter_IFC #(numeric type n);
```

The interface is now parameterized by 'n', the bit-width of the x input.

The bit-width of the y input is constrained to  $\log(n)$ , in order to express any shift amount from 0 to n.


In BSV, certain types and type parameters can be *numeric types*.

Note that *numeric types* (which are only meaningful at compile time) are distinct from *numeric values* (which can of course occur at run time). This is why we use the special notation "TLog#(n)" to express a computation in numeric types.

Strictly speaking, TLog#(n) represents the ceiling of the  $\log(n)$ , i.e., an integer number of bits adequate to hold the binary representation of n.
 
# Sequential, iterative n-bit shifter

File: Eg04b\_MicroArchs/src\_BSV/Shifter\_iterative.bsv




- The FSM (and its actions) is implemented using  $n$  BSV rules
- The rules corresponding to  $j=1..(n-2)$  are generated in a for-loop
- `rg_j` is  $\log(\log(n))$  bits wide, since it selects bits  $0..\log(n)-1$  in `y`
- Note: `rg_x << (2**j)` is not a dynamic shift:  $2^{**j}$  is compile-time constant
- BSV is very strict in type-checking—there are no automatic conversions  
The code uses these explicit conversions:


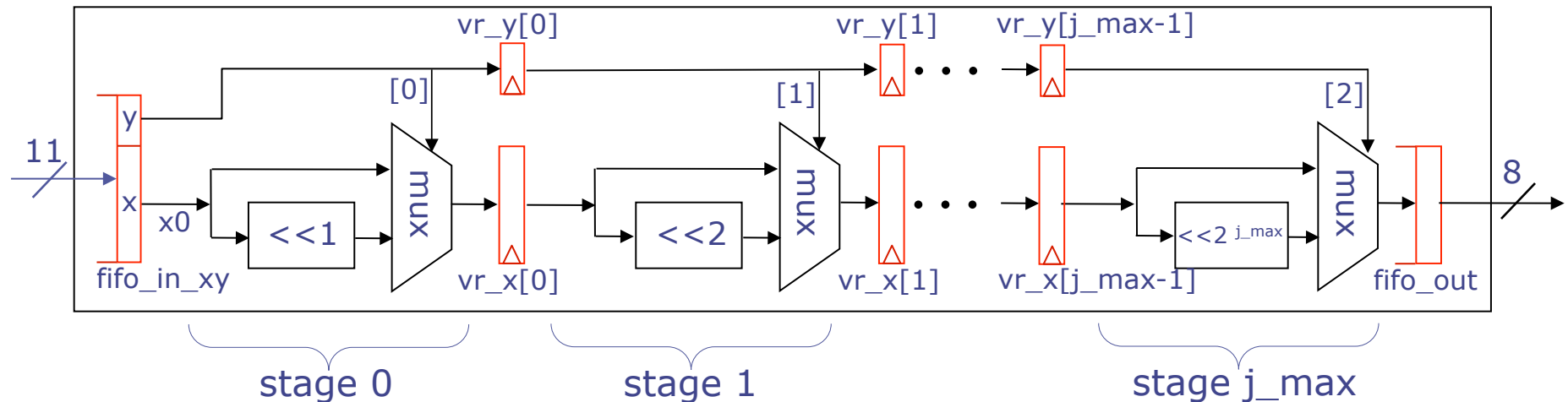
# "Rigid" pipelined n-bit shifter

File: Eg04b\_MicroArchs/src\_BSV/Shifter\_pipe\_rigid.bsv



- The x and y registers are generalized to vectors of  $\log(n)-1$  registers:

```
Vector #(TSub #(TLog #(n), 1), Reg #(Bit #(n)))      vr_x <- replicateM (mkRegU);
Vector #(TSub #(TLog #(n), 1), Reg #(Bit #(TLog #(n)))) vr_y <- replicateM (mkRegU);
```


- The Actions of stages 1..j\_max-1 are generated using a for-loop:

```
rule rl_all_together;
  // Stage 0
  ...
  // Stage j: 1..j_max-1
  vr_x[j] <= ((vr_y[j-1][j] == 0) ? vr_x[j-1]: (vr_x[j-1] << (2**j)));
  vr_y[j] <= vr_y[j-1];

  // Stage j_max
  ...
endrule
```
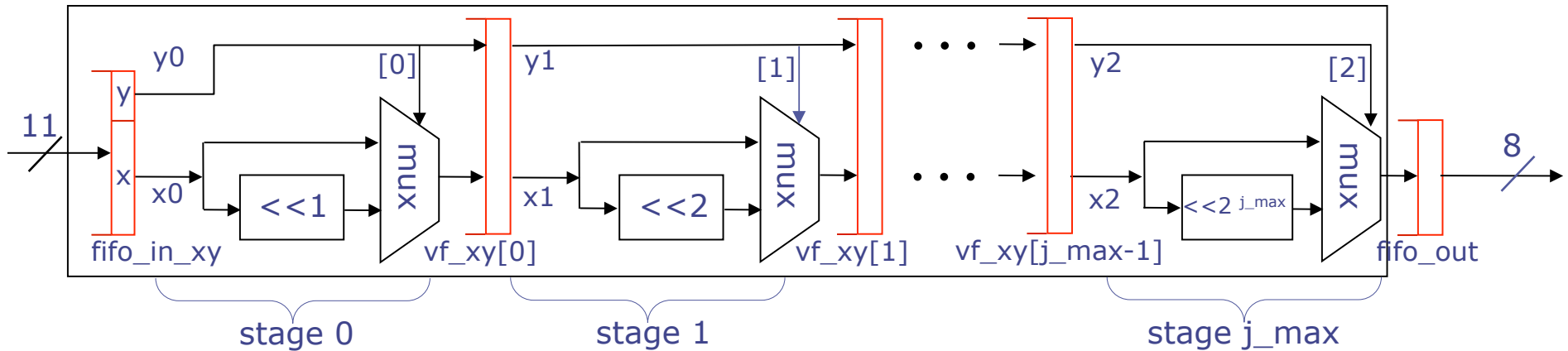
# Elastic, pipelined n-bit shifter

File: Eg04b\_MicroArchs/src\_BSV/Shifter\_pipe\_elastic.bsv



- The xy FIFOs are generalized to *vectors* of  $\log(n)-1$  FIFOs:

```
Vector #(TSub #(TLog #(n), 1),
        FIFO #(Tuple2 #(Bit #(n),
                        Bit #(TLog #(n)))) vf_xy <- replicateM (mkFIFO);
```

- The Rules for stages  $1..j\_max-1$  are generated using a for-loop:

```
for (Integer j = 1; j < j_max; j = j + 1)
  rule r1_j;
    match { .x1, .y1 } = vf_xy[j-1].first; vf_xy[j-1].deq;
    vf_xy[j].enq (tuple2 ((y1[j] == 0) ? x1 : (x1 << (2**j))), y1);
  endrule
```

# Synthesis hierarchy

- In the original 8-bit shifters (in Eg04a\_MicroArchs/ directory), in front of each 'module' line, there is a (\*synthesize\*) attribute:

```
(* synthesize *)  
module mkShifter (Shifter_IFC);  
...  
endmodule
```

- When generating Verilog, this creates a 'mkShifter.v' file with a 'mkShifter' Verilog module
- In the generalized n-bit shifters (in Eg04b\_MicroArchs/ directory), these (\*synthesize\*) attribute are removed.
- This is because BSV cannot separately synthesize *polymorphic* modules; they can only be inlined into a parent module
- Instead, in Testbench.bsv, we have created a specific instance of the module (for shifting 16-bit values); since this is no longer polymorphic, it can be separately synthesized. This is the module actually instantiated in the module mkTestbench:

```
(* synthesize *)  
module mkShifter_16_4 (Shifter_IFC #(16));  
  let m <- mkShifter;  
  return m;  
endmodule
```

- The above is a common idiom in BSV code, for creating a separately synthesized instance of a polymorphic module



## Build and run the generalized shifters

- Build and run the generalized shifters (in Eg04b\_MicroArchs/ directory) in a similar manner to how you ran the 8-bit shifters (in Eg04a\_MicroArchs/ directory)
- Verify that the behaviors are as expected (including the throughputs)


## Suggested exercises

- Change the program to *rotate*  $x$  by  $n$  bits, instead of shifting, i.e., instead of losing bits at the MSB end and shifting in zeroes at the LSB end, the MSB bits should be shifted in at the LSB end.
- Change any one of the `mkShifter` modules so that it takes a *static* boolean parameter such that:
  - If True, we get a circuit that performs left-shifting.
  - If False, we get a circuit that performs left-rotation.
  - (Note: this is a fixed-function circuit, either left-shifting or left-rotation, chosen at compile time.)
- Change any one of the *pipelined* `mkShifter` modules so that it can perform left- and right-shifting and left- and right-rotation, selected dynamically.
  - Change the interface so that the input is now a 3-tuple, where the new, third component is an “opcode” specifying left/right shift/rotate. Define an enum type for this opcode. Note: successive 3-tuple inputs may carry different opcodes, i.e., different pipeline stages may be performing different operations at the same time.
  - (Note: this circuit is a piece of a full-blown “ALU” for a CPU.)

# Summary

- These variations on a “dynamic shifter” illustrate how BSV can be used to express a range of micro-architectures, from FSMs to rigid/synchronous pipelines to elastic/asynchronous pipelines
- They also show how architectures can be parameterized flexibly

# bluespec

 

## End

```

import P2P000;
typedef Bit[24] (outT);
module ex_hdl_csrR_hdl {empty};

Integer nfa_depth = 16;

function Bit[24] distribute_pump(outT out);
return (out);
endfunction

P2P000(outT) in_bond0;
in_bond0.P2P000(nfa_depth) the_in_bond0(in_bond0);
P2P000(outT) out_bond0;
out_bond0.P2P000(nfa_depth) the_out_bond0(out_bond0);
P2P000(outT) out_bond0;
out_bond0.P2P000(nfa_depth) the_out_bond0(out_bond0);

rule exp1 (True);
outT in_data = in_bond0.first;
P2P000(outT) out_data =
distribute_pump(in_data) == 0 ? out_bond0 : out_bond0;
out_data.P2P000(nfa_depth) the_out_data(out_data);
endrule;
endmodule;

```

